

1. A battery has two terminals, a negative and a positive, they are connected with a wire. What type of particles will flow through the wire and which direction will they go?

Electrons, negative to positive

2. A charge of 1800 coulombs was passed through a wire in 2.0 minutes. What was the average current in that interval?

$$I = \frac{Q}{t} = \frac{1800}{120} = 15 \text{ amps}$$

2 × 60 = 120 sec  
↙

3. A steady current of 0.50 A flows through a wire. How many electrons pass through a point in the wire each second?

$$\frac{0.50 \text{ coulombs}}{\text{sec}} \times \frac{2.5 \times 10^{19} \text{ electrons}}{1 \text{ C}} = \frac{1.3 \times 10^{19} \text{ electrons}}{\text{sec}}$$

4. A current of 3.60 A flows for 15.3 s through a conductor. Calculate the number of electrons that pass through a point in the conductor in this time.

$$3.60 \text{ A} = \frac{3.60 \text{ C}}{\text{sec}} \times \frac{15.3 \text{ sec}}{1} \times \frac{2.5 \times 10^{19} \text{ electrons}}{1 \text{ C}}$$
$$= 1.4 \times 10^{21} \text{ electrons}$$

5. How long would it take  $2.0 \times 10^{20}$  electrons to pass through a point in a conductor if the current was 10.0 A?

$$2.0 \times 10^{20} \text{ electrons} \times \frac{1 \text{ coulomb}}{2.5 \times 10^{19} \text{ electrons}} \times \frac{1 \text{ sec}}{10 \text{ coulombs}}$$
$$= 0.80 \text{ seconds}$$

6. A current of 2.0 A flows through a  $28 \Omega$  load. What is the potential difference (voltage) across the load?

$$R = \frac{V}{I} \rightarrow V = RI$$
$$= 28 \Omega \times 2 \text{ A}$$
$$= \textcircled{56 \text{ V}}$$

7. The potential difference across a load is 4.9 V and the current passing through the load is 0.25 A. What is the resistance of the load?

$$R = \frac{V}{I} = \frac{4.9\text{V}}{0.25\text{A}} = 19.6\ \Omega$$
$$\approx 2.0 \times 10^1\ \Omega$$

8. What current will flow through a 250  $\Omega$  load if it has a potential difference of 120 V across it?

$$I = \frac{V}{R} = \frac{120\text{V}}{250\ \Omega} = 0.48\text{A}$$

9. A 9.0 volt battery is connected to a load. What will the current be through the load if
- a. The resistance of the load is 50.0  $\Omega$

$$I = \frac{V}{R} = \frac{9.0\text{V}}{50\ \Omega} = 0.18\text{A}$$

- b. The resistance of the load is 100.0  $\Omega$

$$\frac{9.0\text{V}}{100\ \Omega} = 0.090\text{A}$$


10. A battery is connected to a  $7.0 \Omega$  and  $9.0 \Omega$  load in series. The current through the whole circuit is  $1.3$  amps.

- a. What is the potential difference across the  $9 \Omega$  load?

$$V = IR = 11.7 \text{ V} = 12 \text{ V}$$

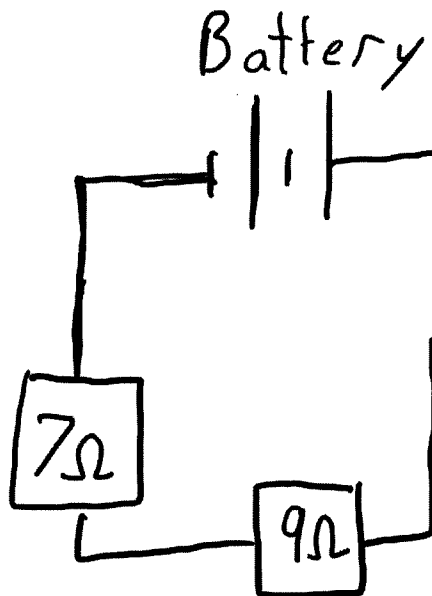- b. What is the potential difference across the  $7 \Omega$  load?

$$1.3 \text{ A} \times 7.0 \Omega = 9.1 \text{ V}$$




11. A battery is connected to a  $3.0 \text{ ohm}$ , and a  $7.0 \text{ ohm}$  load in parallel. The voltage across each load is  $5.9$  volts.

- a. What is the current passing through the  $3 \text{ ohm}$  load?

$$I = \frac{V}{R} = 2.0 \text{ A}$$

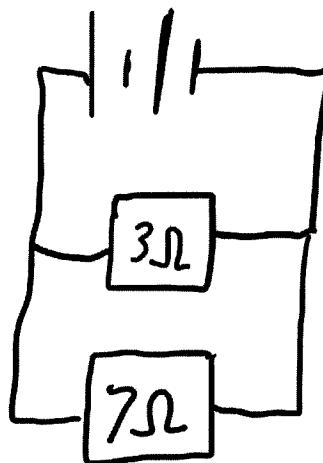- b. What is the current passing through the  $7 \text{ ohm}$  load?

$$\frac{5.9 \text{ V}}{7.0 \Omega} = 0.84 \text{ A}$$



12. A 25 watt lightbulb is connected to a 120 volt power source. What current passes through the lightbulb?

$$P = VI \rightarrow \frac{P}{V} = I$$
$$\frac{25W}{120V} = 0.21A$$

13. A current of 5.0 A passes through a load which is drawing 150 watts of power. What is the potential difference across the load?

$$P = VI \rightarrow \frac{P}{I} = V$$
$$\frac{150W}{5.0A} = 3.0 \times 10^1 V$$

14. A 1600 watt appliance is connected to a 120 volt power source, how much current is it drawing?

$$I = \frac{P}{V} = 13.33$$
$$\approx 13A$$

15. A microwave connected to 120 V power source draws 9.2 amps of power.

a. How much power does it draw?

$$P = VI = 120V \times 9.2A$$

$$= 1104 \approx \text{1100 watts}$$

b. How much energy in joules does it use in 15 seconds?

$$P = \frac{W}{t} \rightarrow W = Pt$$

$$= 1104W \times 15 \text{ sec}$$

$$= \text{17000 J}$$

16. An electric motor is connected to 240 volt power source, it draws 4.5 amps of current. How fast will the motor be able to lift a 500.0 kg object if it is 100% efficient?

$$P = VI = 240V \times 4.5A = 1080 \text{ watts}$$

$$P = Fv \rightarrow \frac{P}{F} = v$$

$$\begin{aligned} \uparrow \\ F_g = mg \\ = 500 \times 9.8 \\ = 4900 \text{ N} \end{aligned}$$

$$\frac{1080 \text{ watts}}{4900 \text{ N}} = \text{0.22 m/s}$$

17. An electric heating element has a resistance of  $85\Omega$ , it is connected to a  $6.0\text{V}$  battery.
- a. What current passes through the heating element?

~~$I = \frac{P}{V}$~~   $I = \frac{V}{R} = \frac{6.0\text{V}}{85\Omega}$

$$= 0.071\text{amps}$$

- b. What is the power the heating element is drawing?

Option 1

$$P = VI$$
$$= 6.0 \times 0.071$$
$$= 0.42\text{watts}$$

Option 2

$$P = \frac{V^2}{R} = \frac{6^2}{85} = 0.42\text{watts}$$

- c. How much energy does the element use in 25 seconds?

$$Pt = E$$

$$0.42 \times 25 = \textcircled{11\text{J}}$$