

1) Currents of 0.25 A and 0.95 A flow through the primary and secondary coils of a transformer respectively, if there are  $1.0 \times 10^3$  turns in the primary coil how many turns are in the secondary coil?

$$\frac{N_p}{N_s} = \frac{I_s}{I_p} \rightarrow \frac{1.0 \times 10^3}{?} = \frac{0.95}{0.25}$$

$$1.0 \times 10^3 \times 0.25 \div 0.95 = \textcircled{260 \text{ turns}}$$

2) A step-down transformer has coils of  $1.20 \times 10^3$  and  $1.5 \times 10^2$  turns. The transformer is connected to a 120 volt power line, and the current in the secondary coil is 5.00 A. What is the current in the primary coil?

$$\frac{N_p}{N_s} = \frac{I_s}{I_p} \rightarrow \frac{1.20 \times 10^3}{1.5 \times 10^2} = \frac{5.00 \text{ A}}{?}$$

$$1.5 \times 10^2 \times 5 \div 1.20 \times 10^3 = \textcircled{0.63 \text{ A}}$$

Step down

so voltage decreases from primary to sec, so more loops in primary

3) Near your home the voltage of the power line is 3600 V. The transformer between your home and the line reduces this voltage to 120 V. If the transformer is to deliver 2400 J of energy each second to your house, what is the current in:

a) the primary coil

$$\frac{2400}{3600} = 0.67 \text{ A}$$

$$\text{Power} = I \times V$$

$$\frac{P}{V} = I$$

b) the secondary coil

$$\frac{2400}{120} = 20 \text{ A}$$

4) A step-down transformer ( $N_p = 150$ ,  $N_s = 25$ ) is connected to a 120 V primary line. If there is a  $75\Omega$  electrical device placed in the secondary circuit, what is the current in the primary coil?

$$\frac{N_p}{N_s} = \frac{V_p}{V_s} \rightarrow \frac{150}{25} = \frac{120}{?} \rightarrow V_s = 25 \times 120 \div 150 = 20V$$

$$I_s = \frac{V}{R} = \frac{20}{75} = 0.2667A$$

$$\frac{150}{25} = \frac{0.2667}{?} \rightarrow I_p = 0.044A$$

5) If the voltage and current of the primary coil is 120 V and 3.0 A, what is the power delivered to the secondary coil?

Power is same in each

$$\text{so } P_s = P_p = VI = 120 \times 3 = 360 \text{ Watts}$$

6) If the power delivered to the secondary coil of a step-up transformer is 50.0 from a 120 V power line, what is the current in the primary coil?

Power is same  
in each

$$P = VI$$

$$\frac{P}{V} = I$$

$$\frac{50 \text{ watts}}{120V} = I = 0.42A$$

7) A transformer ( $N_p = 550$ ,  $N_s = 36$ ) is connected to a 120 V power line. If the current in the <sup>Secondary</sup> primary coil is 1.0 A, what is the ~~power~~ <sup>power</sup> in the secondary coil?

~~Voltage, current and power~~

~~Power is same in each s~~

$$\frac{550}{36} = \frac{I_s}{I_p}$$

$$\frac{550}{36} = \frac{1}{?} \rightarrow I_p = 36 \times 1 \div 550$$

$$= 0.06545$$

$$\text{Power} = \textcircled{7.85 \text{ W}}$$

8) A 100 W transformer ( $N_s = 1500$ ) has an input voltage of 9.0 V and an output current of 0.65 A. How many turns are on the primary coil?

Since it is 100W we can calculate  
Current in primary

$$P = IV$$

$$\frac{P}{V} = I \rightarrow \frac{100}{9} = 11.11 \text{ A}$$

$$\frac{I_s}{I_p} = \frac{N_p}{N_s} \rightarrow \frac{0.65}{11.11} = \frac{?}{1500}$$

$$N_p = 0.65 \times 1500 \div 11.11$$

$$= \textcircled{88 \text{ loops}}$$

100

1000

10000

100000

1000000

10000000

100000000

1000000000

10000000000

100000000000